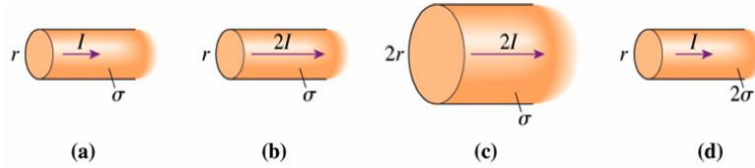



1. Rank in order, from largest to smallest, the current densities  $J_a$  to  $J_d$  in these four wires, which carry currents ranging from  $I$  to  $2I$ .

- a.  $J_b = J_d > J_a > J_c$
- b.  $J_b > J_a > J_c > J_d$
- c.  $J_b > J_a = J_d > J_c$
- d.  $J_c > J_b > J_a > J_d$
- e.  $J_c > J_b > J_a = J_d$



2. A wire carrying a current  $I$  has two equal length segments that have equal diameters. If the conductivities of the material in the two segments have a ratio  $\sigma_1:\sigma_2=2:1$ , what is the ratio  $E_1:E_2$  of the electric field strengths in the two segments of the wire.

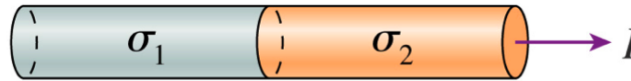- a.  $E_1:E_2=4:1$
- b.  $E_1:E_2=2:1$
- c.  $E_1:E_2=1:1$
- d.  $E_1:E_2=1:2$
- e.  $E_1:E_2=1:4$



3. What is the ratio of the change in potential  $\Delta V_1:\Delta V_2$ ?

- a.  $\Delta V_1: \Delta V_2=4:1$
- b.  $\Delta V_1: \Delta V_2 =2:1$
- c.  $\Delta V_1: \Delta V_2=1:1$
- d.  $\Delta V_1: \Delta V_2=1:2$
- e.  $\Delta V_1: \Delta V_2=1:4$

4. What is the ratio of the resistances  $R_1:R_2$ ?

- a.  $R_1: R_2=4:1$
- b.  $R_1: R_2 =2:1$
- c.  $R_1: R_2=1:1$
- d.  $R_1: R_2=1:2$
- e.  $R_1: R_2=1:4$

5. What is the ratio of the power dissipated in each segment  $P_1:P_2$ ?
- $P_1:P_2=4:1$
  - $P_1:P_2=2:1$
  - $P_1:P_2=1:1$
  - $P_1:P_2=1:2$
  - $P_1:P_2=1:4$
6. Two light bulbs operate on the same potential difference. Bulb A has four times the power output of bulb B. Which bulb has the greater current?
- Bulb A
  - Bulb B
  - Neither - they both have the same current

There is a potential difference of 2.5 V between opposite ends of a 6.0 m long iron wire.  
Note: there is a table with resistivities in Wolfson.

- a) Assuming a uniform electric field in the wire, what is the current density?
- b) If the wire diameter is 1.0 mm, what is the total current?

The maximum safe current in 12-gauge (1.2 mm diameter) copper wire is 20 A.


- a) What is the maximum current density?
- b) What is the maximum electric field?

Engineers call for a power line with a resistance per unit length of  $50 \text{ m}\Omega/\text{km}$ .

- a) What wire diameter is required if the line is made of copper?
- b) What wire diameter is required if the line is made of aluminum?
- c) If the costs of copper and aluminum wire are  $\$4.65/\text{kg}$  and  $\$2.30/\text{kg}$ , respectively, which material is more economical? The densities of copper and aluminum are  $8.9 \text{ g/cm}^3$  and  $2.7 \text{ g/cm}^3$ , respectively.


1. If a large resistor and a small resistor are connected in parallel, the equivalent resistance will be closer in value to that of the:
  - a. large resistor
  - b. small resistor
  - c. Neither; it will be exactly between the two values
  - d. None of the above

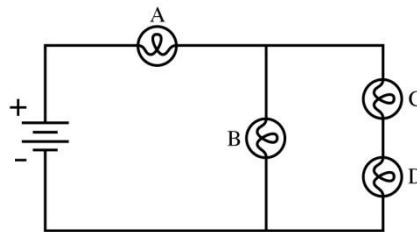2. Refer to the diagram. When the switch is closed the total power dissipated in the circuit will:
  - a. increase
  - b. decrease
  - c. remain the same
  - d. None of the above






© 2004 Pearson Education, Inc., publishing as Addison Wesley

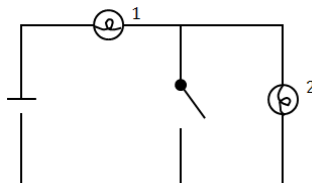3. Rank in order, from brightest to dimmest, the identical bulbs A to D.
  - a.  $A = B = C = D$
  - b.  $A > B > C = D$
  - c.  $A > C > B > D$
  - d.  $A > C = D > B$
  - e.  $C = D > B > A$



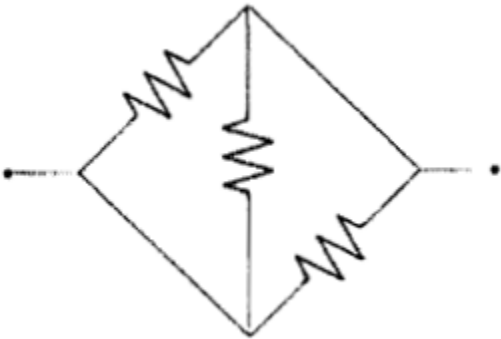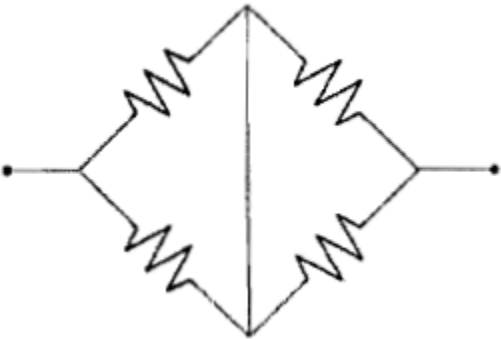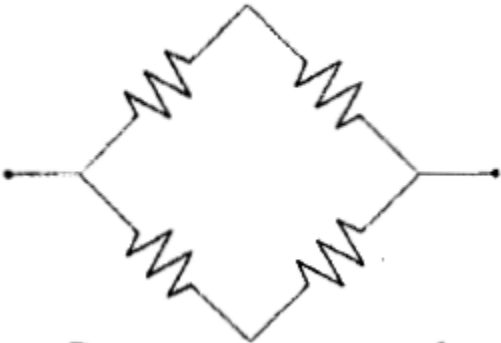
Find the equivalent resistance of the following systems. All resistors have a resistance R.




In this circuit,  $R_1 = 1.0 \text{ k}\Omega$ ,  $R_2 = 3.0 \text{ k}\Omega$ ,  $R_3 = 2.0 \text{ k}\Omega$ , and  $\Delta V = 30 \text{ V}$

Find the:

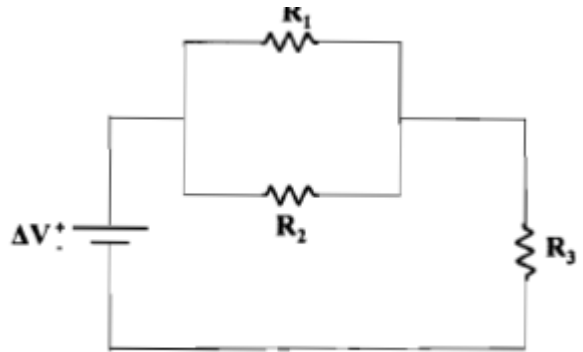- a) Equivalent Resistance
- b) Total Current delivered by the battery
- c) Voltage across each resistor
- d) Power dissipated by each resistor
- e) Total power dissipated in the circuit.



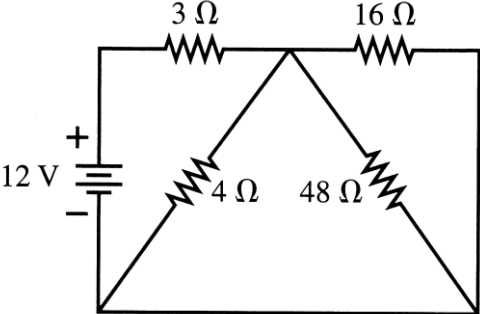For the circuit shown in the figure, find the current through and the potential difference across each resistor.





Wolfson, 25.37

Wolfson 25.42